



Name: \_\_\_\_\_  
Student Number: \_\_\_\_\_  
Lab Section: \_\_\_\_\_  
Instructor: \_\_\_\_\_  
Lab Partner: \_\_\_\_\_

Date: \_\_\_\_\_

## ENG 1450 Introduction to Electrical and Computer Engineering Lab 4 - RC Circuit

### Required equipment:

The equipment required for this lab exercise includes:

- Project board
- Digital multimeters (DMM)
- Oscilloscope
- Function generator
- Capacitors:  $C1 = 1\ \mu\text{F}$  and  $C2 = 470\ \text{nF}$
- Resistors:  $R1 = 1\ \text{k}\Omega$  and  $R2 = 2.2\ \text{k}\Omega$

### RC Circuit Waveforms

Build the circuit shown in Figure 1 for  $R = R1 = 1\ \text{k}\Omega$  and  $C = C1 = 1\ \mu\text{F}$ . For the input voltage  $V_{in}$  use function generator to make a square wave with frequency of 100 Hz and minimum and maximum voltages of 0 V and 5 V, respectively. Use the oscilloscope to find the voltage of the capacitor and plot it on Table 1. Use the Ohm's law to find current  $i$ . Record your results in Table 1. Use the oscilloscope to find the voltage of the capacitor,  $V_c$ , and record your result in Table 1.

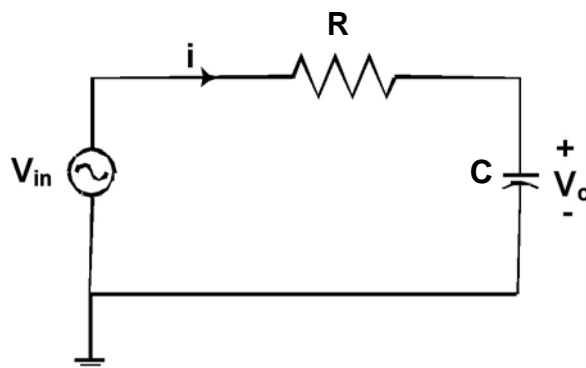


Figure 1: RC circuit.

Table 1: Case 1:  $\mathbf{R} = R1 = 1\text{ K}\Omega$ ,  $\mathbf{C} = C1 = 1\text{ }\mu\text{F}$ , and frequency = 100 Hz

<b>Input</b>	<b>5V</b>				
	<b>0V</b>				
<b>V<sub>C</sub></b>					
<b>i</b>					

Describe how you can find the time constant of the RC circuit based on your experimental results.  
What is the time constant?

$$\tau = \text{-----s}$$

What is the theoretical time constant of the circuit shown in Figure 1?

$$\tau = \text{-----s}$$

Repeat this experiment for the following cases and measure the capacitor voltage.

Table 2: Case 2:  $\mathbf{R} = R1 = 1\text{ K}\Omega$ ,  $\mathbf{C} = C2 = 470\text{ nF}$ , and frequency = 100Hz

<b>Input</b>	<b>5V</b>				
	<b>0V</b>				
<b>V<sub>C</sub></b>					

Table 3: Case 3:  $\mathbf{R} = R2 = 2.2\text{ K}\Omega$ ,  $\mathbf{C} = C1 = 1\text{ }\mu\text{F}$ , and frequency = 100Hz

<b>Input</b>	<b>5V</b>				
	<b>0V</b>				
<b>V<sub>C</sub></b>					

Table 4: Case 4:  $R = R_2 = 2.2 \text{ K}\Omega$ ,  $C = C_1 = 470 \text{ nF}$ , and frequency = 100 Hz

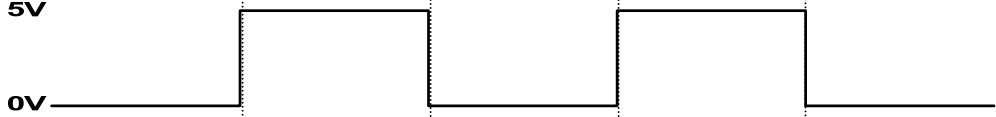

<b>Input</b>	<div> <div>5V</div> <div>0V</div>  </div>
<b>V<sub>C</sub></b>	<div>  </div>

Table 5: Case 5:  $R = R_1 = 1 \text{ K}\Omega$ ,  $C = C_1 = 1 \mu\text{F}$ , and frequency = 50 Hz

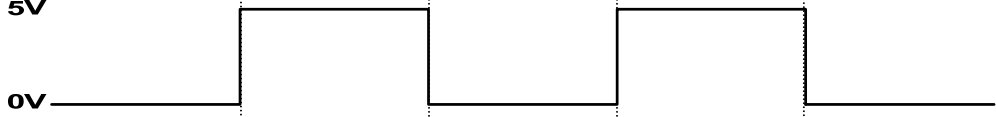

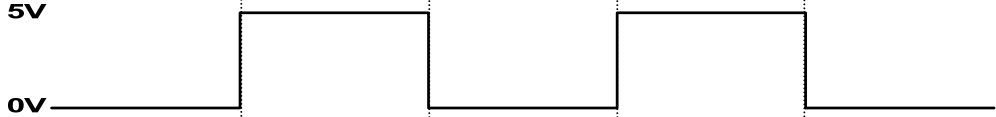

<b>Input</b>	<div> <div>5V</div> <div>0V</div>  </div>
<b>V<sub>C</sub></b>	<div>  </div>

Table 6: Case 6:  $R = R_1 = 1 \text{ K}\Omega$ ,  $C = C_1 = 1 \mu\text{F}$ , and frequency = 200 Hz

<b>Input</b>	<div> <div>5V</div> <div>0V</div>  </div>
<b>V<sub>C</sub></b>	<div>  </div>

Compare the time constant in case 1 with that in cases 2 - 6 and complete the following table.

	Time constant has ... (circle one)	By looking at the <b>V<sub>C</sub></b> curve, explain why the time constant has increased, decreased or remained the same.
Case 2	increased decreased remained the same	
Case 3	increased decreased remained the same	
Case 4	increased decreased remained the same	
Case 5	increased decreased remained the same	
Case 6	increased decreased remained the same	