



DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE No.: 1 of 1
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi

INSTRUCTIONS:

- Do not remove the staple.
 - Closed-book exam. No books/notes allowed.
 - Electronic devices (such as calculators, PDAs, iPods, etc.) are NOT allowed.
 - This is a multiple choice examination and consists of 30 questions.
 - Mark your answer in pencil on the bubble sheet provided.
 - Return both this booklet and the bubble sheet at the end of the examination.
 - No marks will be given for working on this booklet.
 - Each correct answer has one mark and each wrong answer has zero marks.
 - No negative marks for wrong answer.
 - A formula sheet is provided on the last page.
-

STUDENT NUMBER

PRINT YOUR NAME IN FULL ON THIS LINE

SIGNATURE

A01 (Prof. Shafai) A02 (Prof. Kordi)

CIRCLE YOUR SECTION

E2-229 EITC U College – Great Hall

CIRCLE EXAMINATION CENTRE

SEAT NUMBER

Mark	
Out of	30



DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 2 of 2
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi

1 Consider a resistive circuit with DC voltage/current sources. Which of the following is incorrect?


- A) If the circuit has only one source, the source provides power.
- B) If the circuit has only one source, the total power absorbed by all the resistors is equal to the power provided by the source.
- C) If the circuit has two or more sources, there might be a source that absorbs power.
- D) If the circuit has two or more sources, at least one of them provides power.
- E) None of the above.

2 In a DC circuit (a circuit with DC sources only), there is a resistor in series with a capacitor. The circuit has been connected for a long time. Which of the following is incorrect?

- A) The current of the resistor is zero.
- B) The voltage of the resistor is zero.
- C) The power absorbed by the resistor is zero.
- D) The energy stored in the capacitor is equal to the energy absorbed by the resistor.
- E) None of the above.


3 Which of the following is correct?

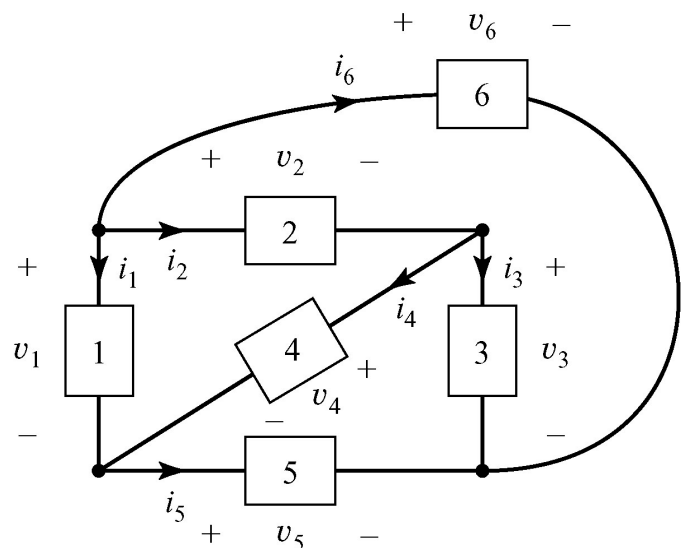- A) $i_1 + i_2 = i_6$
- B) $i_1 + i_2 = 0$
- C) $i_1 + i_2 = i_3 + i_5$
- D) $i_1 + i_2 = i_4$
- E) None of the above.



4 What is the value of $v_w + v_y$ in the circuit shown below?

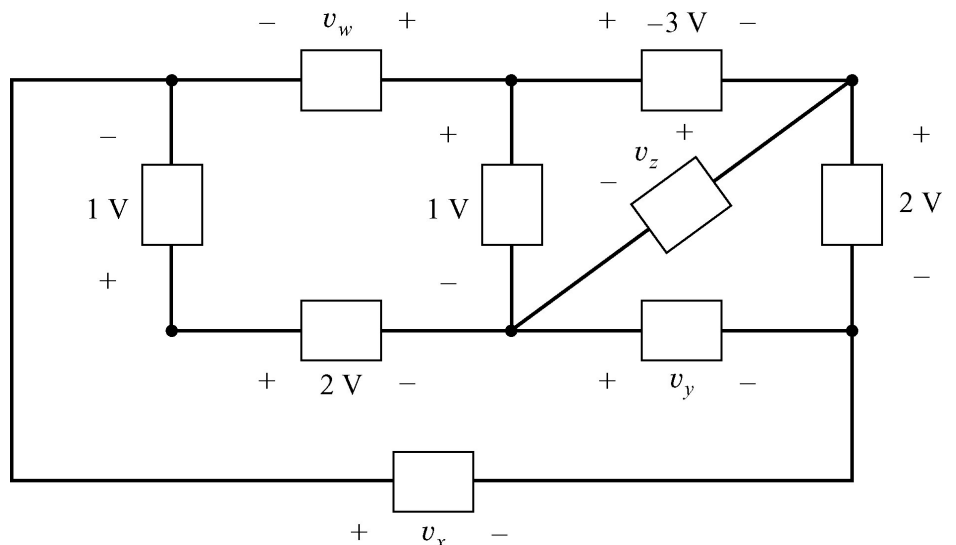- A) 2 V
- B) -2 V
- C) 3 V
- D) -3 V
- E) 0 V






DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 3 of 3
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi

5 How much is the total power absorbed by all the resistors?

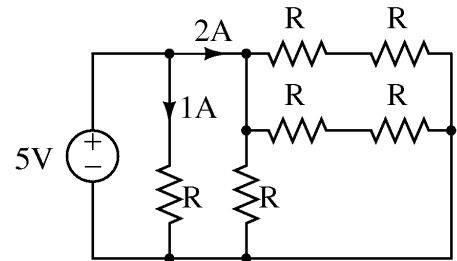- A) 5 W
- B) 10 W
- C) 15 W
- D) 20 W
- E) Not enough information is provided.




6 What is the value of R in Problem 5?

- A) 5 Ω
- B) 10 Ω
- C) 15 Ω
- D) 20 Ω
- E) Not enough information is provided.


7 If the power of the component shown below is -5 W, then the voltage V is equal to...

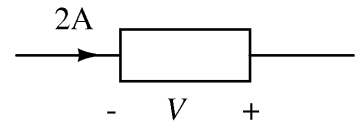- A) +10 V
- B) -2.5 V
- C) +2.5 V
- D) -1.25 V
- E) None of the above.



8 Which of the following is correct for the circuit shown below?

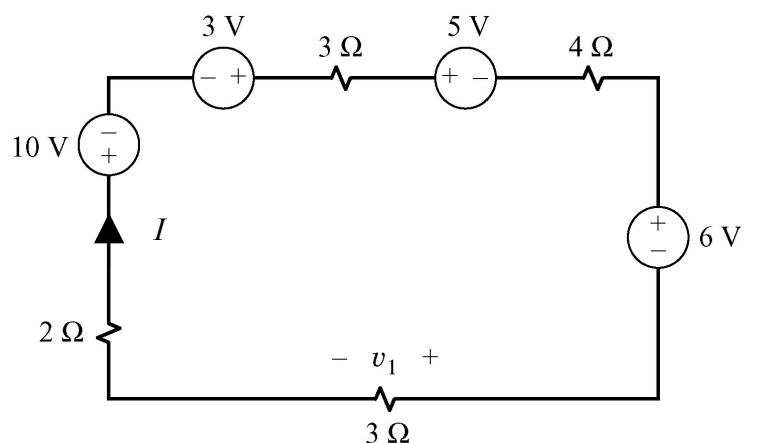- A) All four voltage sources deliver power.
- B) The current of the loop, I , is 1.5 A.
- C) The voltage v_1 is 4.5 V.
- D) The power absorbed by any of the 3- Ω resistors 4.5 W.
- E) None of the above.





DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours


DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 4 of 4
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi

9 What is the power absorbed by the 4-Ω resistor in the circuit of Problem 8?

- A) 0 W
- B) 6 W
- C) 8 W
- D) 9 W
- E) 16 W


10 What are i_x and i_y , respectively?

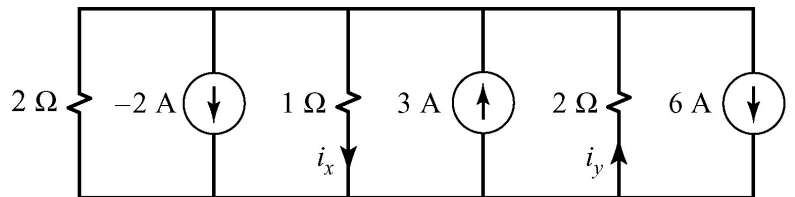- A) + 0.5 A, + 0.25 A
- B) + 0.5 A, - 0.25 A
- C) - 0.5 A, + 0.25 A
- D) - 0.5 A, - 0.25 A
- E) None of the above.




11 A current source is connected to four identical and parallel 2-Ω resistors, as shown below. If the power absorbed by each resistor is 2 W, how much is the value of the current source?

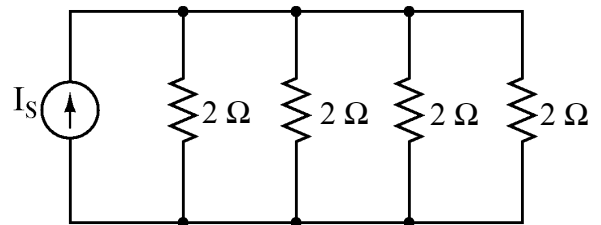- A) + 1 A
- B) - 1 A
- C) + 4 A
- D) - 4 A
- E) Both C and D.




12 In the circuit given below, we have $v_1 = 2v_2 = 3v_3$ and $R_1 = 6 \Omega$, then $R_1 + R_2 + R_3$ is equal to...

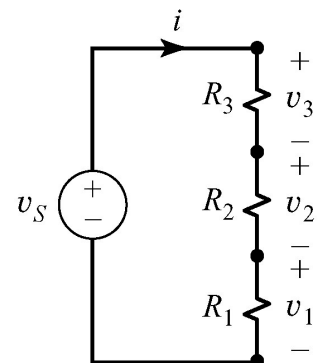- A) 18 Ω
- B) 11 Ω
- C) 36 Ω
- D) 12 Ω
- E) None of the above.



13 What is the voltage V in the circuit shown below?

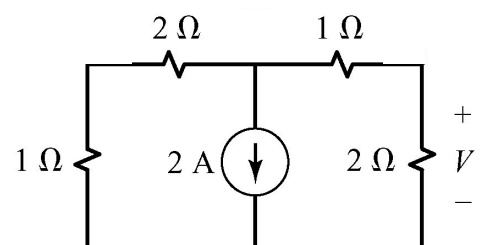- A) -4 V
- B) +4 V
- C) -2 V
- D) +2 V
- E) None of the above.






DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 5 of 5
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi


14 What is the voltage V in the circuit shown below?

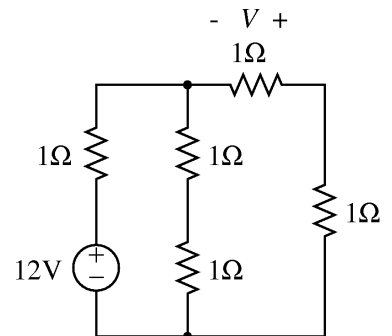- A) -2.4 V
- B) $+2.4 \text{ V}$
- C) -6 V
- D) $+3 \text{ V}$
- E) -3 V




15 15 identical resistor are connected as shown below. If the equivalent resistance at terminals ab is 15Ω , the value of each resistor is...

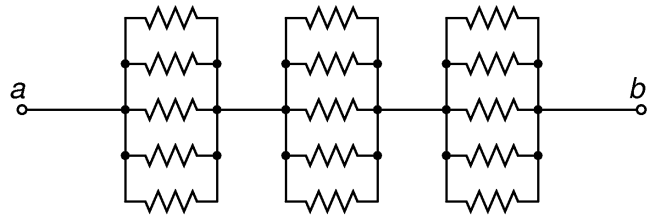- A) 25Ω .
- B) 9Ω .
- C) 1Ω .
- D) 10Ω .
- E) not an integer number.



16 In the circuit shown below, if each of the $4\text{-}\Omega$ resistors is replaced by a $2\text{-}\Omega$ resistor the equivalent resistance at terminals ab ...

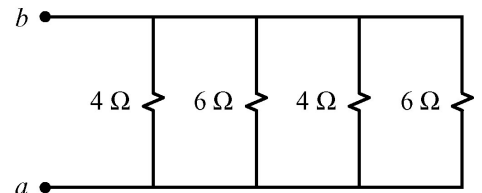- A) increases by $2/15 \Omega$.
- B) decreases by $2/15 \Omega$.
- C) increases by $9/20 \Omega$.
- D) decreases by $9/20 \Omega$.
- E) doesn't change.




17 The equivalent capacitance of ten identical capacitors that are connected in parallel is $20 \mu\text{F}$. If we connect them in series the equivalent resistance is equal to...

- A) $2 \mu\text{F}$.
- B) 200 nF .
- C) 20 nF .
- D) $20 \mu\text{F}$.
- E) none of the above.

18 The circuit shown below has been connected for a long time. How much is the energy stored in the inductor?

- A) 2 J
- B) 4 J
- C) 0 J

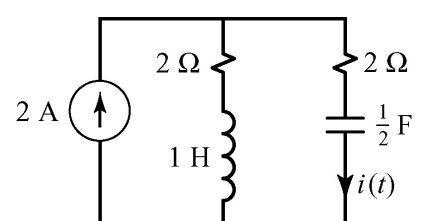



DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 6 of 6
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi

- D) 1.5 J
E) None of the above.


I

19 What is the impedance of a 10-nF capacitor at $\omega = 100$ rad/s?

- A) $j 10^{-6} \Omega$
B) $-j 10^6 \Omega$
C) $-j/(2\pi) \text{ M}\Omega$
D) $-j 500/\pi \text{ k}\Omega$
E) None of the above

20 The current of a 2-H inductor is $i(t) = 5\sin(2t+30^\circ)$. What is the voltage of the inductor?

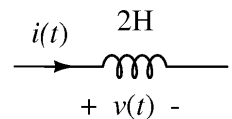- A) $v(t) = 10\sin(2t-60^\circ) \text{ V}$
B) $v(t) = 5\sin(2t+90^\circ) \text{ V}$
C) $v(t) = 10\sin(2t+120^\circ) \text{ V}$
D) $v(t) = 20\sin(2t+120^\circ) \text{ V}$
E) None of the above.



21 What is the binary representation of $(16\text{DEC}10)_{16}$?

- A) 1011011011110110000010000
B) 1011011011110111000010000
C) 1010011011110110000010000
D) 1011111011110110000010000
E) 1011011011110110000110000

22 What is the minimum number of bits needed for the unsigned binary representation of $(511)_{10}$?

- A) 7
B) 8
C) 9
D) 10
E) 11

23 The 6-bit binary representation of $(-23)_{10}$ using 1's complement is given by...

- A) 010111
B) 110111
C) 101001
D) 101111
E) 101000

24 An 8-bit computer that uses 2's complement is used to evaluate $(-25) + (+23)$. Which of the following is calculated by the computer as the answer?

- A) 00000010
B) 11111101
C) 01111110
D) 11111110



DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 7 of 7
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi

E) None of the above.

25 An 8-bit computer uses 2's complement to store negative numbers. The range of numbers that can be stored in this computer is...

- A) from -256 to +256
- B) from -127 to +127
- C) from -255 to +256
- D) from -128 to +127
- E) none of the above.

26 Which of the following does show the truth table for $z = x' + y$?

A)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

B)

x	y	z
0	0	1
0	1	0
1	0	0
1	1	1

C)

x	y	z
0	0	1
0	1	0
1	0	0
1	1	0


D)

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

E)

x	y	z
0	0	1
0	1	1
1	0	0
1	1	1

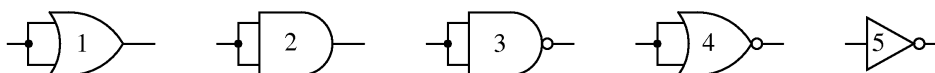27 Which of the following statements is correct?



- A) Digital circuits 1 and 4 are equivalent.
- B) Digital circuits 2 and 3 are equivalent.
- C) Digital circuits 3 and 5 are equivalent.
- D) Digital circuits 1 and 5 are equivalent.
- E) Digital circuits 2 and 5 are equivalent.




DEPARTMENT: Electrical & Computer Engineering
COURSE NO: ENG 1450
COURSE TITLE: Intro. Electrical & Computer Eng.
DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800
PAGE NO.: 8 of 8
EXAMINATION: Final (50%)
EXAMINERS: C. Shafai/B. Kordi


28 Which of the following describes the following digital circuit?

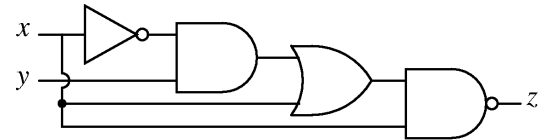- A) $z = x' \cdot y + x \cdot x'$
B) $z = (x' \cdot y + x \cdot x)'$
C) $z = (x' \cdot y + x) \cdot x'$
D) $z = [(x' \cdot y + x) \cdot x]'$
E) None of the above.



29 Which of the following is correct for the circuit shown below?

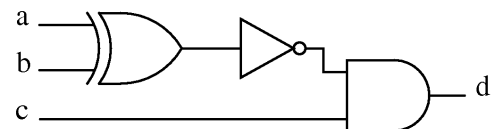- A) If $a=b=c=0$, then $d=1$.
B) If $a=b=c=1$, then $d=0$.
C) If $a=b=0$ and $c=1$, then $d=1$.
D) If $a=1$ and $b=c=0$, then $d=1$.
E) None of the above.



30 The digital variables x and y show if the two front doors of a car are open or not (0: open, 1: closed). The output of a digital circuit, z , controls a light (0: off, 1: on). The circuit must turn the light on when either of (but not both) doors are open. Which of the following does describe the operation of this circuit?

A)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

B)

x	y	z
0	0	1
0	1	0
1	0	0
1	1	1

C)

x	y	z
0	0	1
0	1	0
1	0	0
1	1	0

D)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 16th December 2010 at 1800

COURSE NO: ENG 1450

PAGE NO.: 9 of 9

COURSE TITLE: Intro. Electrical & Computer Eng.

EXAMINATION: Final (50%)

DURATION: 2 Hours

EXAMINERS: C. Shafai/B. Kordi

E)

<i>x</i>	<i>y</i>	<i>z</i>
0	0	1
0	1	1
1	0	1
1	1	0

Formula Sheet

Ohm’s law:	$V = RI$
Power:	$P = VI$
Voltage division:	$V_k = \frac{R_k}{\sum R_i} V_S$
Current division:	$I_k = \frac{\frac{1}{R_k}}{\sum \frac{1}{R_i}} I_S$
Resistors in series:	$R_{eq} = \sum R_i$
Resistors in parallel:	$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$
Capacitors in series:	$\frac{1}{C_{eq}} = \sum \frac{1}{C_i}$
Capacitors in parallel:	$C_{eq} = \sum C_i$
Inductors in series:	$L_{eq} = \sum L_i$
Inductors in parallel:	$\frac{1}{L_{eq}} = \sum \frac{1}{L_i}$
Energy stored in a capacitor:	$W = \frac{1}{2} CV^2$
Energy stored in an inductor:	$W = \frac{1}{2} LI^2$
Impedance of a capacitor:	$Z_C = \frac{1}{j\omega C}$, where $\omega = 2\pi f$
Impedance of an inductor:	$Z_L = j\omega L$, where $\omega = 2\pi f$

α	0°	30°	45°	60°	90°	120°	135°	150°	180°
----------	----	-----	-----	-----	-----	------	------	------	------



DEPARTMENT: Electrical & Computer Engineering

COURSE NO: ENG 1450

COURSE TITLE: Intro. Electrical & Computer Eng.

DURATION: 2 Hours

DATE & TIME: 16th December 2010 at 1800

PAGE NO.: 10 of 10

EXAMINATION: Final (50%)

EXAMINERS: C. Shafai/B. Kordi

$\sin \alpha$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{1}{2}$	0
$\cos \alpha$	1	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{1}{2}$	0	$-\frac{1}{2}$	$-\frac{\sqrt{2}}{2}$	$-\frac{\sqrt{3}}{2}$	-1
$\tan \alpha$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	∞	$-\sqrt{3}$	-1	$-\frac{\sqrt{3}}{3}$	0