



DEPARTMENT:	Electrical & Computer Engineering	DATE & TIME:	1 st November 2010 at 1800
PAPER NO.:	—	PAGE NO.:	1 of 5
COURSE:	ENG 1450–Intro. Elect. & Comp. Eng.	EXAMINATION:	Mid-term (20%)
DURATION:	1 Hour	EXAMINERS:	C. Shafai/B. Kordi

INSTRUCTIONS:

- Do not remove the staple.
 - Closed-book exam. No books/notes allowed.
 - Calculators are NOT allowed.
 - Return both this booklet and the bubble sheet at the end of the examination.
 - This is a multiple choice examination and consists of 15 questions.
 - Mark your answer in pencil on the bubble sheet provided.
 - No marks will be given for working on this booklet.
 - Each correct answer has one mark and each wrong answer has zero marks.
 - No negative marks for wrong answer.
-

STUDENT NUMBER

PRINT YOUR NAME IN FULL ON THIS LINE

SIGNATURE

A01 (Prof. Shafai) A02 (Prof. Kordi)

CIRCLE YOUR SECTION

E2-105 E2-110 E3-270

CIRCLE YOUR EXAMINATION ROOM

(n/a)

SEAT NUMBER

Mark	
Out of	15



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 1st November 2010 at 1800

PAPER NO.: —

PAGE NO.: 2 of 5

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.

EXAMINATION: Mid-term (20%)

DURATION: 1 Hour


EXAMINERS: C. Shafai/B. Kordi

- 1 A 10-V battery has been supplying power to a flashing light for 10 hours. The flashing light is on for 1 second and is off for 2 seconds, in a repeating cycle. If the resistance of the light (when it is on) is $10\ \Omega$, then how much energy has been supplied by the battery for every 30-minute period of time?

- A) 3,000 J.
B) 6,000 J.
C) 12,000 J.
D) 36,000 J.
E) 120,000 J.


- 2 In the circuit shown below, what is $\frac{i_x}{i_w}$?

- A) 2.
B) 1.
C) 0.
D) -1.
E) -2.

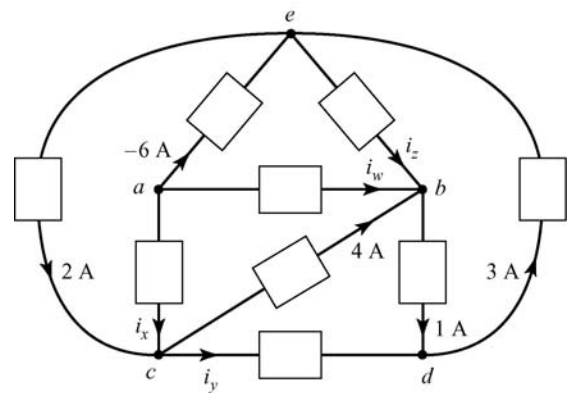


- 3 What is $v_u + v_y$ in the circuit shown below?

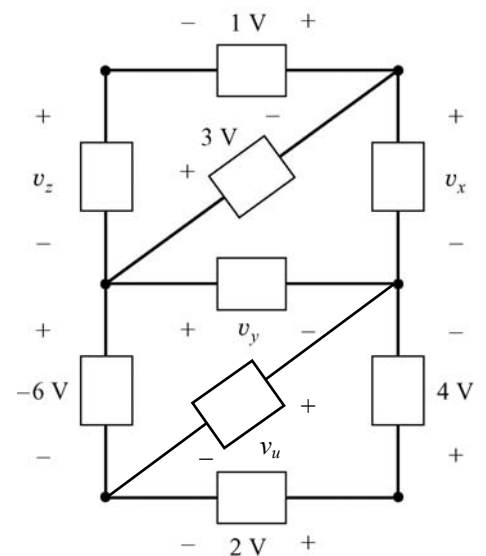- A) 2 V.
B) 4 V.
C) 6 V.
D) -6 V.
E) None of the above.



- 4 How much power is delivered/absorbed by the 3-V voltage source?

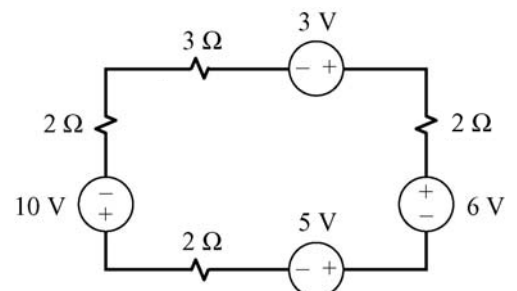- A) 6 W, delivered.
B) 6 W, absorbed.
C) 18 W, delivered.
D) 18 W, absorbed.
E) -6 W, absorbed.





DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 1st November 2010 at 1800

PAPER NO.: —

PAGE NO.: 3 of 5

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.

EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: C. Shafai/B. Kordi

5 How much is the total power absorbed by all resistors in the circuit of Problem 4?


- A) 0 W.
- B) 18 W.
- C) 36 W.**
- D) 162 W.
- E) None of the above.

6 We have an unknown number of identical resistors. When we connect them in series the equivalent resistance is $100\ \Omega$, and when we connect them in parallel the equivalent resistance is $1\ \Omega$. How many resistors do we have and what is the resistance of each of them?

- A) 4 resistors, $25\ \Omega$ each.
- B) 10 resistors, $1\ \Omega$ each.
- C) 10 resistors, $10\ \Omega$ each.**
- D) 5 resistors, $20\ \Omega$ each.
- E) None of the above.


7 What is the equivalent resistance at terminals ab ?

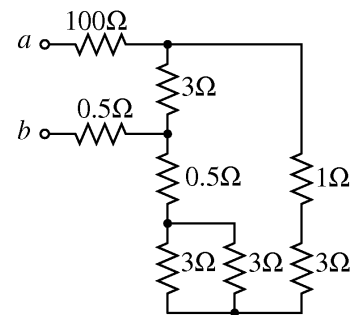- A) $103.5\ \Omega$.
- B) $114\ \Omega$.
- C) $106\ \Omega$.
- D) $102.5\ \Omega$.**
- E) None of the above.




8 What is $\frac{v_y}{v_x}$ in the circuit shown below?

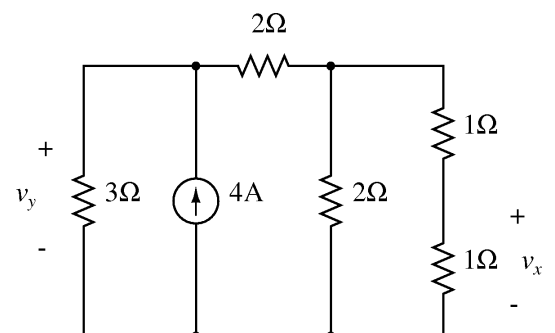- A) 6.**
- B) 5.
- C) 4.
- D) 3.
- E) None of the above.



9 Determine the value of R so that $v_x = 5\text{ V}$.

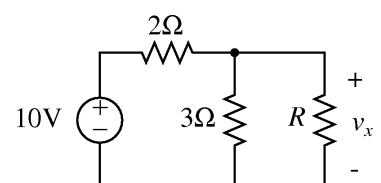- A) $6\ \Omega$.**
- B) $3\ \Omega$.
- C) $2\ \Omega$.
- D) $1\ \Omega$.
- E) None of the above.





DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 1st November 2010 at 1800

PAPER NO.: —

PAGE NO.: 4 of 5

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: C. Shafai/B. Kordi


10 How much power is absorbed/delivered by the 3-A current source?

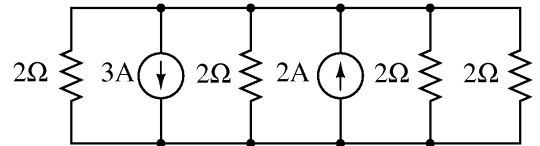- A) 2.5 W, delivered.
- B) 1.5 W, delivered.**
- C) 0.5 W, delivered.
- D) 0.5 W, absorbed.
- E) None of the above.




11 How much power is absorbed by the 3-Ω resistor?

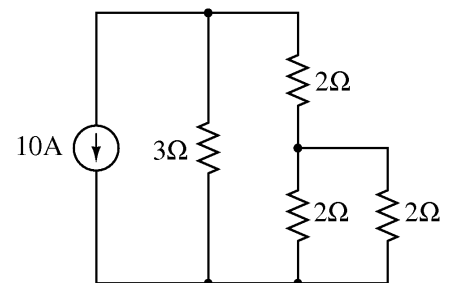- A) 15 W.
- B) 100/3 W.
- C) 75 W.**
- D) 100 W.
- E) None of the above.



12 What is the current i_x in the circuit given below?

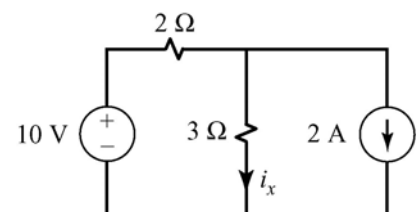- A) 2 A.
- B) 3 A.
- C) -1.2 A.
- D) 1.2 A.**
- E) None of the above.



13 What is the capacitance of a capacitor that can store 18 mJ when charged by a 6-V voltage?

- A) 10 mF.
- B) 1000 μF.**
- C) 1 F.
- D) 10,000 nF.
- E) None of the above.




DEPARTMENT: Electrical & Computer Engineering
PAPER NO.: —
COURSE: ENG 1450–Intro. Elect. & Comp. Eng.
DURATION: 1 Hour

DATE & TIME: 1st November 2010 at 1800
PAGE NO.: 5 of 5
EXAMINATION: Mid-term (20%)
EXAMINERS: C. Shafai/B. Kordi


14 For what values of V_S , R_f , and R_i the output voltage of the following circuit, V_{out} , is -12 V?

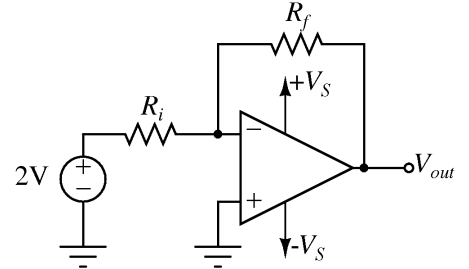- A) $V_S = 10$ V, $R_f = 10$ Ω , $R_i = 10$ Ω .
B) $V_S = 10$ V, $R_f = 60$ Ω , $R_i = 10$ Ω .
C) $V_S = 15$ V, $R_f = 10$ Ω , $R_i = 60$ Ω .
D) $V_S = 12$ V, $R_f = 10$ Ω , $R_i = 10$ Ω .
E) None of the above.



15 A wire carries an electric current, I , that is flowing in the $+y$ direction as shown below. What is the direction of the magnetic field generated by this current at point A?

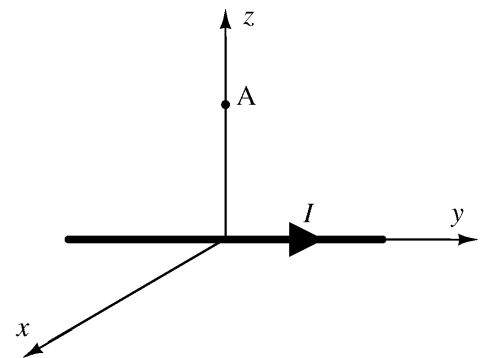- A) $+y$.
B) $+x$.
C) $-x$.
D) $+z$.
E) $-z$.



Formula Sheet

Ohm's law

$$V = RI$$

Power

$$P = VI$$

Energy

$$\text{Energy} = \text{Power} \times \text{Time}$$

Voltage division

$$V_k = \frac{R_k}{\sum R_i} V_S$$

Current division

$$I_k = \frac{\frac{1}{R_k}}{\sum \frac{1}{R_i}} I_S$$

Resistors in series

$$R_{eq} = \sum R_i$$

Resistors in parallel

$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$$

Energy stored in a capacitor

$$W = \frac{1}{2} CV^2$$