



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 1 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.

EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: S. Sherif/J. Cai

INSTRUCTIONS:

- Write your full name, student number, and lecture section on both this test paper and the bubble sheet.
- Do not remove the staple.
- Closed-book exam. No books/notes allowed.
- Non-programmable calculators are allowed.
- Return both this booklet and the bubble sheet at the end of the examination.
- This is a multiple choice examination and consists of 15 questions.
- Mark your answer in pencil on the bubble sheet provided.
- No marks will be given for working on this booklet.
- Each correct answer has one mark and each wrong answer has zero marks.
- No negative marks for wrong answer.

STUDENT NUMBER

PRINT YOUR NAME IN FULL ON THIS LINE

SIGNATURE

A01 (Prof. Sherif) A02 (Prof. Cai)

CIRCLE YOUR SECTION

E2-105 E2-165 E3-270

CIRCLE YOUR EXAMINATION ROOM

(n/a)

SEAT NUMBER

Mark	
Out of	15



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 2 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.

EXAMINATION: Mid-term (20%)

DURATION: 1 Hour


EXAMINERS: S. Sherif/J. Cai

- 1 What does the halogen gas in a halogen incandescent lamp do?
- A) Coats the tungsten filament and prevents it evaporating quickly.
 - B) Re-deposits evaporated tungsten back on the filament.
 - C) Cools the filament so it lasts longer.
 - D) Makes the light brighter by absorbing infrared light from the filament and converting it to visible light.
 - E) None of the above.

- 2 If 5×10^{16} electrons are pushed by the energy of 20 mJ, what is the voltage? (Each electron carries a negative charge equal to -1.6×10^{-19} C.)
- A) 4 V
 - B) 12.5 V
 - C) 2.5 V
 - D) 1 V
 - E) None of the above


- 3 What is the value of V_c ?

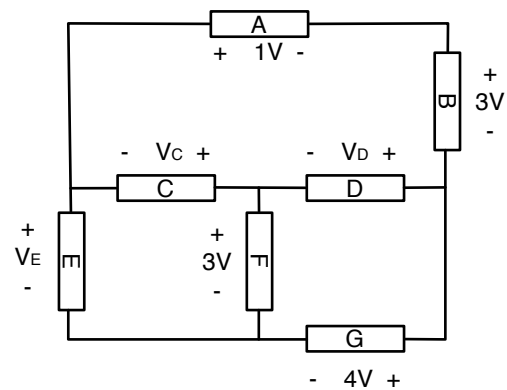- A) 5 V
- B) 3 V
- C) -4 V
- D) -5 V
- E) -3 V



- 4 In the given circuit, what is the value of V_{ab} ?

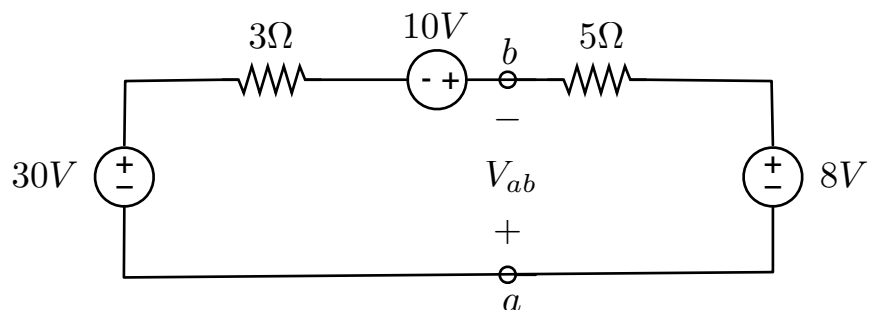- A) 28 V
- B) -28 V
- C) 12 V
- D) -12 V
- E) 20 V





DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 3 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: S. Sherif/J. Cai


5 How much power is delivered/absorbed by the 3V voltage source?

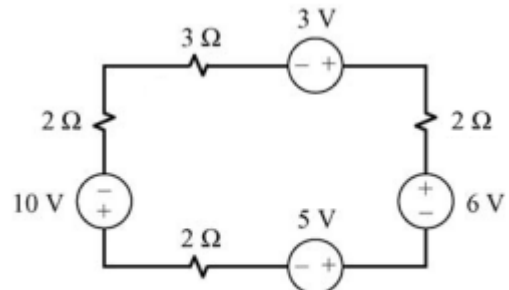- A) 6 W, delivered.
- B) 6 W, absorbed.
- C) 18 W, delivered.
- D) 18 W, absorbed.
- E) -6 W, absorbed.




6 For the given circuit, what is the value of i ?

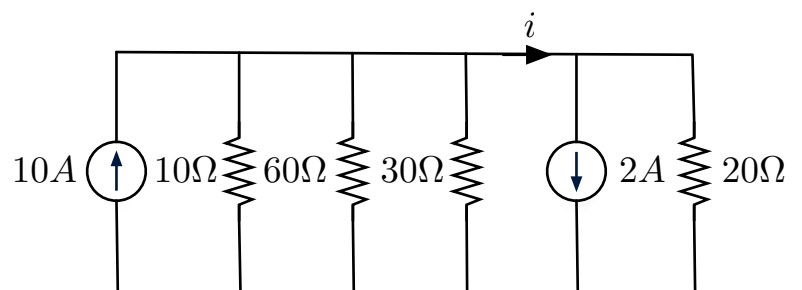- A) 4 A
- B) 3 A
- C) 2 A
- D) 1 A
- E) None of the above



7 What is the equivalent resistance at terminals ab ?

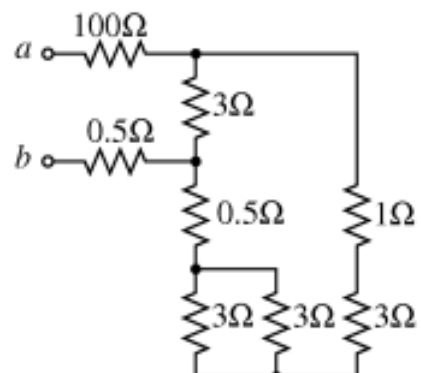- A) 103.5 Ohms
- B) 114 Ohms
- C) 106 Ohms
- D) 102.5 Ohms
- E) None of the above.





DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 4 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: S. Sherif/J. Cai


8 In the given circuit, what is the value of I ?

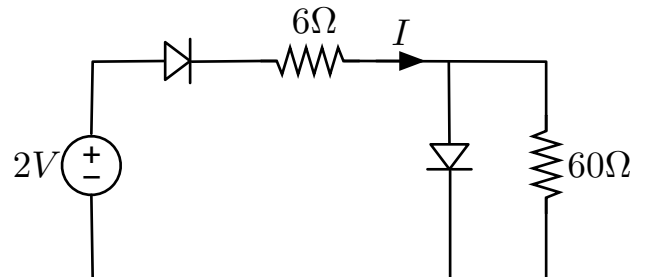- A) 0.1 A
- B) 0.3 A
- C) -1 A
- D) 0.03 A
- E) None of the above




9 What are the values of v_x and i_x in the given circuit?

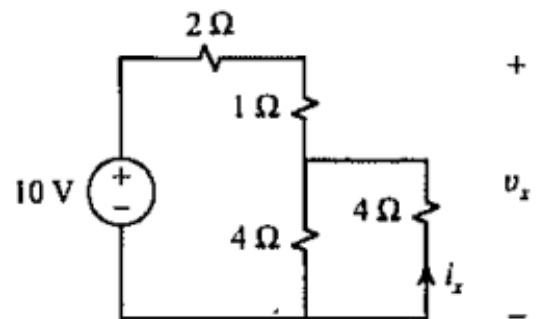- A) 4 V and -1 A
- B) -6 V and 1 A
- C) 4 V and -1 A
- D) 4 V and 1 A
- E) 6 V and -1 A



10 What is the current I in the given circuit?

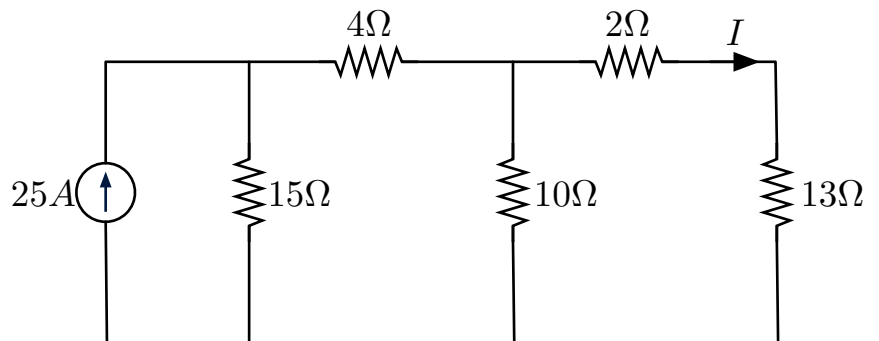- A) 0.8 A
- B) 2.6 A
- C) 9 A
- D) 6 A
- E) None of the above





DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 5 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: S. Sherif/J. Cai


11 How much power is absorbed by the 3 Ohms resistor?

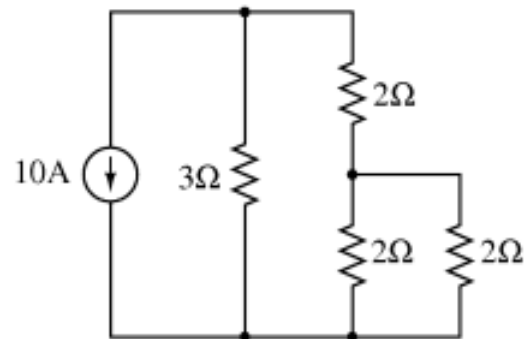- A) 15 W.
- B) $100/3$ W.
- C) 75 W.
- D) 100 W.
- E) None of the above.



12 In the given circuit, what is the value if i_1 ?

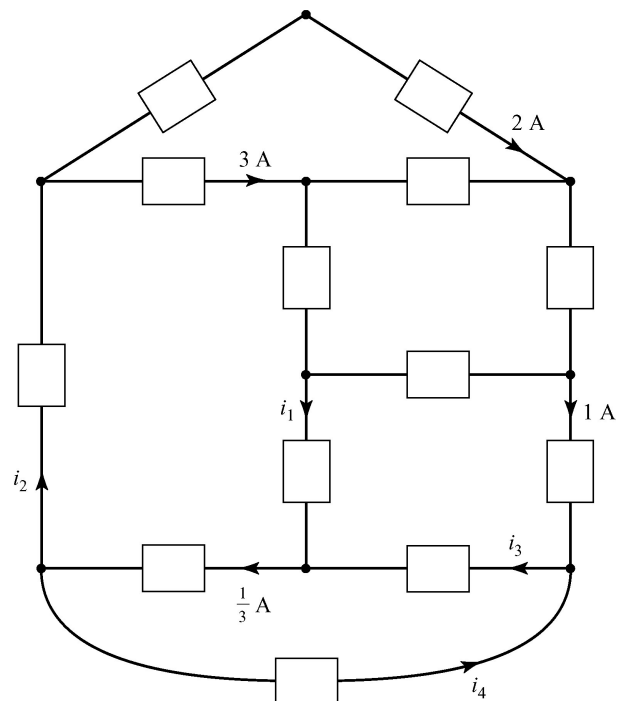- A) 1 A
- B) 3 A
- C) -1 A
- D) 2 A
- E) 4 A





DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 6 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.


EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: S. Sherif/J. Cai


- 13 A wire carries an electric current, I , that is flowing in the $+y$ direction as shown below. What is the direction of the magnetic field generated by this current at point A?

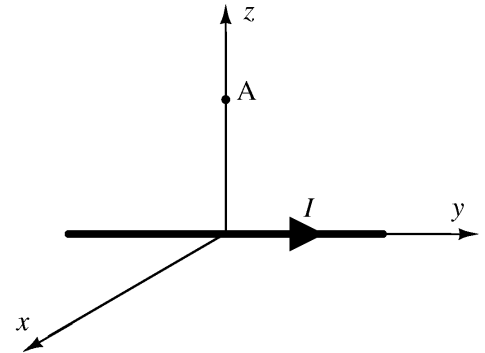- A) $+y$
- B) $+x$
- C) $-x$
- D) $+z$
- E) $-z$




- 14 In the given circuit, what is the energy stored in 3H inductor at the steady state?

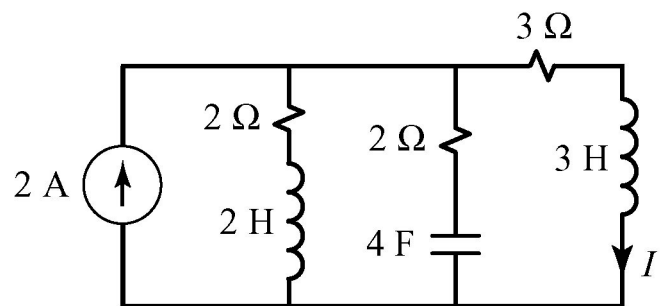- A) 3.375 J
- B) $2/3$ J
- C) 0.96 J
- D) 0 J
- E) None of the above



- 15 Determine the equivalent capacitance C_{eq} .

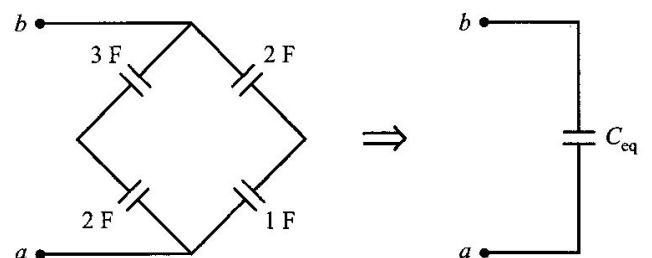- A) $C_{eq} = 1.875$ F
- B) $C_{eq} = 2.22$ F
- C) $C_{eq} = 1.8667$ F
- D) $C_{eq} = 2$ F
- E) None of the above





DEPARTMENT:	Electrical & Computer Engineering	DATE & TIME:	4 th March 2014 at 18:30
PAPER NO.:	—	PAGE NO.:	7 of 8
COURSE:	ENG 1450—Intro. Elect. & Comp. Eng.	EXAMINATION:	Mid-term (20%)
DURATION:	1 Hour	EXAMINERS:	S. Sherif/J. Cai

Formula Sheet

Ohm’s law $V=RI$

Power $P=VI$

Energy $W=VQ$

Voltage division $V_k = \frac{R_k}{\sum R_i} V_s$

Current division $I_k = \frac{\frac{1}{R_k}}{\sum \frac{1}{R_i}} I_s$

Resistors in series $R_{eq} = \sum R_i$

Resistors in parallel $\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$

Energy stored in capacitors $W = \frac{1}{2} CV^2$

Energy stored in inductors $W = \frac{1}{2} LI^2$



DEPARTMENT: Electrical & Computer Engineering

DATE & TIME: 4th March 2014 at 18:30

PAPER NO.: —

PAGE NO.: 8 of 8

COURSE: ENG 1450—Intro. Elect. & Comp. Eng.

EXAMINATION: Mid-term (20%)

DURATION: 1 Hour

EXAMINERS: S. Sherif/J. Cai

This page is intentionally left blank.